

Contents

Unit- I : Circuit Analysis Techniques

1.1	Introduction	1.3
1.2	Circuit elements	1.5
1.3	Resistors inductors and capacitors [R–L–C]	1.9
1.3.1	Resistors	1.9
1.3.2	Inductors.....	1.10
1.3.3	Capacitors	1.10
1.4	Voltage current relations for R, L and C	1.11
1.4.1	Resistor.....	1.11
1.4.2	Capacitor.....	1.12
1.4.3	Inductor	1.13
1.5	Phasor form of voltage current relationship of R, L and C	1.14
1.5.1	Resistor.....	1.14
1.5.2	Inductor	1.15
1.5.3	Capacitor.....	1.16
1.6	Energy sources	1.17
1.7	Series connection of independent sources	1.17
1.7.1	Series circuits.....	1.18
1.8	Parallel connection of independent sources	1.19
1.8.1	Parallel circuits	1.20
1.9	Ohm’s law	1.21
1.10	Kirchoff’s Current Law	1.21
1.11	Kirchoff’s Voltage Law	1.23
1.12	Network Theorems	1.25
1.12.1	Thevenin’s Theorem	1.25
1.13	Norton’s Theorem.....	1.28
1.14	Superposition Theorem	1.30
1.15	Maximum power transfer Theorem.....	1.33
1.16	Duality.....	1.39
1.17	Star-delta conversion (or) Transformation.....	1.41
1.17.1	Equivalent star circuit and Delta circuits.....	1.42
1.17.2	Star-delta transformation.....	1.43
1.18	Solved Examples.....	1.47
1.19	For Practice	1.59
	Part-A Question and Answer.....	1.62
	Review Questions	1.67

Unit-II : Transient Resonance in RLC Circuits

2.1	Introduction	2.3
2.2	Waveform	2.3
2.3	RL circuit.....	2.5
2.4	RC circuit	2.6
2.5	RLC circuit.....	2.8
2.6	Power and Energy consumed by Resistor, Inductor & Capacitor	2.11
	2.6.1 Power absorbed by an Resistor	2.11
	2.6.2 Power absorbed by an Inductor.....	2.12
	2.6.3 power absorbed by a Capacitor	2.13
2.7	RL circuit and their response to sinusoidal inputs	2.14
2.8	RC circuit and their response to sinusoidal inputs.....	2.17
2.9	RLC circuit and their response to sinusoidal inputs	2.21
2.10	DC response of an RL circuit	2.24
2.11	DC response of an RC circuit.....	2.28
2.12	DC response of an RLC circuit	2.31
2.13	Resonance.....	2.36
2.14	Series resonance.....	2.37
	2.14.1 Frequency response	2.38
	2.14.2 Phase angle of a Series resonant circuit	2.39
	2.14.3 Impedance and current in a series RLC circuit.....	2.39
	2.14.4 Bandwidth of an RLC circuit	2.42
2.15	Quality factor (Q-factor).....	2.46
2.16	Magnification in resonance.....	2.48
2.17	Parallel resonance	2.49
	2.17.1 Resonant frequency of a tank circuit.....	2.51
2.18	Coupled circuits	2.53
2.19	Mutal inductance	2.54
2.20	Dot convention	2.54
2.21	Co-efficient of coupling	2.55
	2.21.1 Series connection of coupled inductors.....	2.56
	2.21.2 Parallel connection of coupled inductors	2.57
2.22	Tuned circuits	2.59
	2.22.1 Single tuned circuit.....	2.59
	2.22.2 Double tuned coupled circuits.....	2.65
	Part-A Question and Answer.....	2.71
	Review Questions	2.73

Unit-III : Semiconductor Diodes

3.1	Introduction	3.3
3.2	Ideal Diode.....	3.3
3.3	Semiconductors	3.5
3.3.1	Semiconductor Materials.....	3.5
3.3.2	Importance of Si and Ge	3.6
3.3.3	Atomic Structure	3.6
3.4	Classification of Semiconductors.....	3.7
3.4.1	Intrinsic Semiconductor	3.7
3.4.2	Extrinsic Semiconductor.....	3.10
3.4.3	The Mass-action law.....	3.11
3.5	Charge Densities in a Semiconductor	3.12
3.6	Electrical Properties of Ge and Si	3.13
3.6.1	Conductivity and Drift current.....	3.13
3.6.2	Intrinsic concentration	3.14
3.6.3	The mobility.....	3.15
3.7	The Hall effect	3.16
3.8	Carrier Concentration in Intrinsic semiconductor.....	3.18
3.8.1	Donor or N-type and Acceptor or P-type Impurities	3.22
3.9	Drift and diffusion currents	3.23
3.10	Carrier life time.....	3.27
3.11	Continuity Equation	3.29
3.12	Theory of PN Junction Diode	3.31
3.12.1	No applied Bias ($V_D = 0$ V)	3.31
3.12.2	Reverse Bias condition ($V_D < 0$ V)	3.34
3.12.3	Forward Bias condition ($V_D > 0$ V)	3.35
3.12.4	Limiting values of PN junction diode	3.36
3.13	Resistance Levels	3.36
3.13.1	DC or static resistance.....	3.36
3.13.2	AC or Dynamic resistance	3.37
3.13.3	Average AC resistance	3.37

3.14	Diode Equivalent Circuit	3.38
3.14.1	Piecewise linear equivalent circuit	3.38
3.14.2	Simplified equivalent circuit	3.39
3.14.3	Ideal equivalent circuit	3.39
3.15	Energy Band structure of an open circuit PN junction.....	3.40
3.16	Quantitative theory of PN-junction Diode currents.....	3.43
3.16.1	Forward current.....	3.45
3.16.2	Reverse saturation current	3.45
3.16.3	Diode current equation	3.46
3.17	Capacitive Effects in a PN junction diode.....	3.47
3.17.1	C_j in a step -graded junction.....	3.49
3.17.2	Diffusion or Storage Capacitance (C_D)	3.51
3.18	Effect of Temperature on PN junction Diodes	3.54
3.19	Junction Diode Switching Characteristics.....	3.55
3.19.1	Storage time and Transition time	3.55
3.20	Breakdown In PN Junction Diodes.....	3.58
3.21	Zener diodes	3.59
3.21.1	Introduction.....	3.59
3.21.2	Zener Diode.....	3.60
3.21.3	Zener Diode Specification	3.60
3.21.4	Avalanche Breakdown	3.61
3.21.5	Zener Breakdown	3.62
3.21.5	Applications	3.63
3.22	Solved Examples	3.64
	Part-A Questions and Answers.....	3.78
	Review Questions	3.86

Unit-IV - Transistors

4.1	Introduction	4.3
4.2	Transistor construction	4.4
4.2.1	Basic transistor operation	4.5
4.3	Transistor biasing	4.6
4.4	Operation of NPN transistor	4.6
4.4.1	Transistor currents.....	4.7

4.5	Operation of pnp transistor	4.8
4.5.1	Large - signal current gain	4.9
4.5.2	Ggeneral transistor equation	4.9
4.5.3	Relation among I_C , I_B and I_{CBO}	4.9
4.5.4	Relation among I_C , I_B and I_{CEO}	4.10
4.5.5	Relation between I_{CBO} and I_{CEO}	4.11
4.5.6	Expression for Emitter Current.....	4.11
4.5.7	DC current gain	4.11
4.6	Types of Configuration	4.11
4.6.1	The common-base configuration	4.13
4.6.2	The common-emitter configuration.....	4.16
4.6.3	The common-collector configuration	4.19
4.6.4	Current amplification factor.....	4.21
4.6.5	A comparision of CB, CE and CC configuration	4.21
4.6.6	Relationship between α and β	4.22
4.7	Breakdown in transistors	4.23
4.7.1	Avalanche multiplication	4.23
4.7.2	Reach-through	4.25
4.8	Analytical expression for transistor characteristics.....	4.26
4.8.1	Base-spreading resistance	4.26
4.8.2	Ebers-moll model.....	4.27
4.9	Transistor switching times	4.28
4.9.1	A simple application of a transistor switch	4.29
4.10	Field Effect Transistor - Introduction.....	4.33
4.11	Construction of n-channel JFET	4.33
4.11.1	FET characteristics	4.35
4.11.2	Expression for Pinch off voltage and Drain current	4.39
4.11.3	Transfer characteristics.....	4.41
4.12	Characteristic parameters of the JFET	4.43
4.13	Expression for saturation drain current.....	4.45
4.14	Slope of the transfer characteristic at I_{DSS}	4.46
4.15	Comparison between FET and BJT	4.47
4.16	Applications of JFET	4.48
4.17	Metal Oxide Semiconductor Field Effect Transistor (MOSFET) .	4.49
4.17.1	Depletion-Type MOSFET	4.49
4.17.2	Enhancement-Type MOSFET	4.54
4.18	MOSFET handling	4.58
4.19	Comparision of MOSFET with JFET	4.60

4.20	Comparison of n with p- channel MOSFETs	4.61
4.21	Comparison of n with p channel JFETs.	4.61
	Part-A Questions and Answers.....	4.62
	Review Questions	4.81

Unit-V : Special Semiconductor Devices (Qualitative Treatment Only)

5.1	Introduction	5.3
5.1.1	Tunnel diode	5.3
5.1.2	Applications	5.4
5.2	Pin diode.....	5.4
5.3	Backward diode.....	5.5
5.3.1	Varactor diode.....	5.6
5.3.2	Application.....	5.6
5.4	Step recovery diode.....	5.7
5.4.1	Theory	5.7
5.4.2	Uses	5.8
5.5	Laser diode	5.9
5.6	Point - contact diode.....	5.9
5.7	Photoconductive position sensors	5.10
5.7.1	Photo-conductive sensors	5.12
5.7.2	Photoconductive cell.....	5.13
5.8	Junction type photoconductive cell.....	5.14
5.8.1	Phototransistor.....	5.16
5.9	Photovoltaic sensors	5.17
5.9.1	Photovoltaic effect	5.17
5.9.2	Photovoltaic cell	5.17
5.10	Photo emissive sensors	5.18
5.10.1	Vacuum photodiode	5.18
5.10.2	Gas filled phototube.....	5.19
5.10.3	Photomultiplier	5.20
5.11	Light emitters	5.21
5.11.1	Light Emitting Diode (LED)	5.21
5.11.2	Construction of LED	5.23
5.11.3	Advantages of LEDs in electronic displays	5.23
5.11.4	Disadvantages of LEDs	5.24
5.12	Liquid Crystal Displays (LCDs).....	5.24
5.12.1	Characteristics of Liquid Crystal Materials	5.24

5.12.2	Dynamic Scattering Display (DSD).....	5.25
5.12.3	Twisted nematic crystal display.....	5.25
5.12.4	Comparison between LCD and LED displays	5.26
5.13	Nixie tube	5.27
5.14	Alphanumeric displays	5.28
5.15	Opto electronic devices	5.30
5.16	Opto couplers	5.31
5.16.1	Typical parameters.....	5.33
5.16.2	Applications	5.33
5.17	The Silicon Controlled Rectifier (SCR).....	5.33
5.17.1	SCR biasing	5.34
5.17.2	SCR operation.....	5.35
5.17.3	SCR equivalent circuit	5.36
5.17.4	Turning on (or triggering) SCR.....	5.37
5.17.5	Turning off SCR.....	5.38
5.17.6	V-I characteristics of SCR.....	5.38
5.17.7	Forward characteristic	5.39
5.17.8	Reverse characteristic of SCR	5.40
5.17.9	SCR ratings	5.41
5.18	LASCR (Light Activated SCR).....	5.42
5.19	The DIAC and TRIAC.....	5.43
5.19.1	Introduction.....	5.43
5.20	The DIAC (Diode a.c switch)	5.43
5.21	The TRIAC.....	5.45
5.21.1	Introduction.....	5.45
5.21.2	TRIAC operation	5.48
5.21.3	TRIAC applications.....	5.48
5.21.4	Difference between SCR and TRIAC	5.49
5.22	The Uni-Junction Transistor (UJT)	5.49
5.22.1	Introduction.....	5.49
5.22.2	Basic construction of UJT	5.50
5.22.3	Equivalent circuit of UJT	5.50
5.22.4	Stand off ratio.....	5.52
5.22.5	UJT operation	5.52
5.22.6	V-I characteristic of UJT.....	5.53
5.22.7	UJT applications	5.54
5.22.8	UJT relaxation Oscillator	5.54
5.22.9	Frequency of Oscillation	5.56
	Part A Questions and Answers.....	5.57
	Review Questions	5.69

CIRCUITS AND DEVICES LABORATORY

1.	Verification of Kirchoff's Law	Lab. 3
2.	Verification of Thevenin's Theorem.	Lab. 9
3.	Verification of Superposition Theorem	Lab. 15
4.	Verification of Maximum power transfer theorem	Lab. 21
5.	(a) Frequency response of Series resonance circuits.....	Lab. 25
	(b) Frequency response of Parallel resonance circuits.....	Lab. 29
6.	(a) Characteristics of PN Junction diode	Lab. 35
	(b) Characteristics of Zener diode.....	Lab. 39
7.	Characteristics of CE configuration	Lab. 43
8.	Characteristics of UJT	Lab. 49
9.	Characteristics of SCR.....	Lab. 53
10.	Characteristics of JFET	Lab. 57
11.	Characteristics of DIAC	Lab. 63
12.	Characteristics of TRIAC.....	Lab. 67

ANNA UNIVERSITY MODEL QUESTION PAPERS Q.1